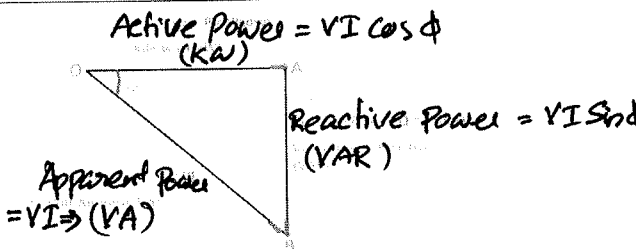
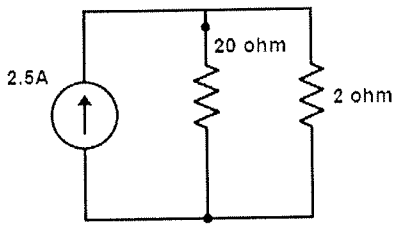
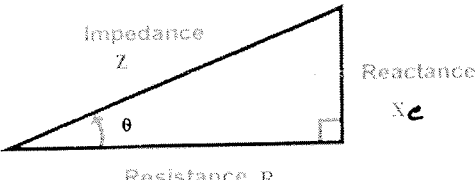



Scoring Indicators

COURSE NAME : Fundamentals of Electric circuits
COURSE CODE : 3033





QID : 2110220135





Q.No.	Scoring Indicators	Split score	Sub Total	Total score
PART A				9
I.1	Open Circuited		1	
I.2	Node		1	
I.3	$A = A < \theta$		1	
I.4	$Z = R - jX_c$ or $Z = \sqrt{R^2 + X_c^2}$		1	
I.5	Minimum current		1	
I.6	<p style="text-align: center;">Active Power = $VI \cos \phi$ (KW)</p>  <p style="text-align: center;">Reactive Power = $VI \sin \phi$ (VAR)</p> <p style="text-align: center;">Apparent Power = $VI \Rightarrow$ (VA)</p>		1	
I.7	i. Admittance method, ii. Vector method		1	
I.8	$I_L = \sqrt{3} I_{ph}$		1	
I.9	Zero		1	
PART B				24
II.1	<p style="text-align: right;"><i>Statement-3 marks</i></p> <p>Maximum power transfer theorem states that the DC voltage source will deliver maximum power to the variable load resistance only when the load resistance is equal to the source impedance. For this circuit the maximum power transferred only when $R_s = R_L$.</p> <p>The maximum power transferred, $P_{max} = \frac{V_{th}^2}{4R_{th}}$</p>	3	3	
II.2	<p style="text-align: right;"><i>Each step- 0.5 marks</i></p> <ol style="list-style-type: none"> 1. Remove the resistance (if any) across the two given terminals and kept the terminal as open circuited. 2. Compute the open circuit voltage, V_{th} 3. Remove all voltage and current sources by short circuiting and open circuiting respectively. 4. Find Thevenin's resistance R_{th}. 5. Draw the thevenin equivalent circuit with V_{th} and R_{th}. 6. Complete the equivalent circuit by connecting 	6*0.5	3	



	the load resistance.			
II.3	<p>Short circuit current-1 mark Norton's resistance-1 mark Current through 2 ohm-1 mark</p> <p>➤ Remove 2Ω and short the terminal ➤ Find the short circuit current, $I_{sc} = 2.5A$ ➤ Find R_N. $R_N = 10 \parallel 10 + 15 = 20\Omega$ ➤ Norton equivalent is</p>  <p>➤ $I_{2\Omega} = 2.27A$</p>	1 1 1	3	
II.4	<p>Impedance triangle-2 mark Terms explanation-1 mark</p> <p><u>Impedance Triangle</u></p>  <p><u>Impedance Z</u> Opposition offered by the elements in an ac circuit is called impedance. $Z = \sqrt{R^2 + X_c^2}$</p> <p><u>Reactance X</u> Opposition offered by inductor or capacitor in an ac circuit. Inductive reactance, $X_L = L\omega$ Capacitive reactance, $X_C = 1/C\omega$</p>	2 1	3	
II.5	<p>three points-1 mark each</p> <p>For a series RLC circuit, 1. Resonance occurs when $X_L = X_C$. At resonance, 2. current is maximum. $I_m = V/R$ 3. Pf is unity</p>	3	3	


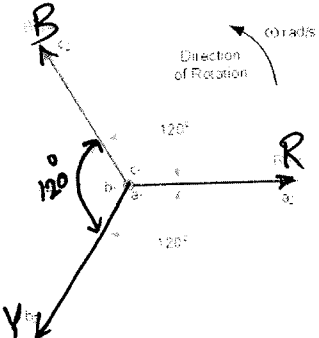
II.6	1 mark for each definition Definitions of Active power, Reactive power and Apparent Power.	3	3	
II.7	Total impedance-2 marks Current-1 mark $Z=Z_1 Z_2$ $Z_1=\sqrt{8^2+7^2}=10.6\Omega$ $Z_2=\sqrt{5^2+6^2}=7.8$ $Z=\frac{Z_1Z_2}{Z_1+Z_2}=4.49$ $I=\frac{V}{Z}=22.27\text{ A}$	2 1	3	
II.8	Defenition-1.5 marks Equation-1.5 marks Q-factor:- the current magnification in the parallel RLC circuit at resonance is called Q-factor. Q-factor= I_0/I Now, $I_c = \frac{V}{X_c} = V\omega C$ $I = \frac{V}{L/\omega C} = \frac{V\omega C}{L}$ Q – factor = $\frac{1}{R}\sqrt{\frac{L}{C}}$	3	3	
II.9	Expressions-1.5 marks Phasor diagram-1.5 marks <u>Voltage equations</u> $E_1=E_m \sin\omega t$ $E_2=E_m \sin(\omega t+120^\circ)$ $E_3=E_m \sin(\omega t-120^\circ)$ <u>Phasor Diagram</u> 	1.5 1.5	3	
	Any 3 points -1 mark each			


II.10	<p>Advantages of three phase systems</p> <ol style="list-style-type: none"> 1. The total power delivered is constant if load is balanced. 2. The output of 3 phase motor is 1.5 times the output of 1 phase motor for a given size. 3. Three phase induction motors are self starting. 4. The efficiency of polyphase motors is greater than single phase motor. 5. Power factor is more than the single phase motor for same rating. 6. Polyphase system is more reliable. <p>Parallel operation of polyphase alternator is simple.</p>	3	3	
PART C				42
III.	<p style="text-align: right;"><i>20 V alone- 3 marks</i> <i>10A alone-3 marks</i> <i>Total current-1 mark</i></p> <p>➤ Consider 20V alone ➤ Remove 10A by open the terminal.</p> <div data-bbox="347 1189 919 1447" data-label="Diagram"> </div> <p>➤ Current through 40 ohm=$20/(15+20+40)=0.266A$ ➤ Consider 10A alone ➤ Remove 20V by shorting its terminal</p> <div data-bbox="360 1630 863 1888" data-label="Diagram"> </div> <p>➤ 20 series 40=60 ➤ Current dividing rule, $I' = -2A$ ➤ By super position principle, current through 40 ohm=$0.266-2 = -1.73A$</p>	3	7	

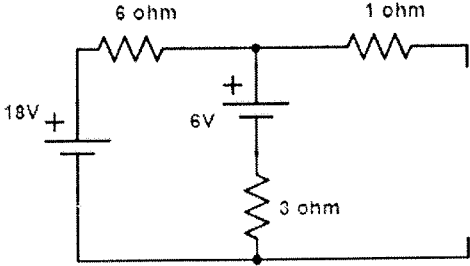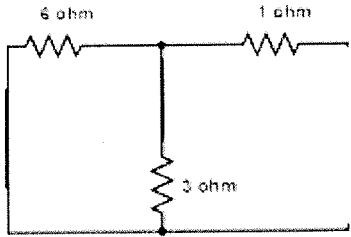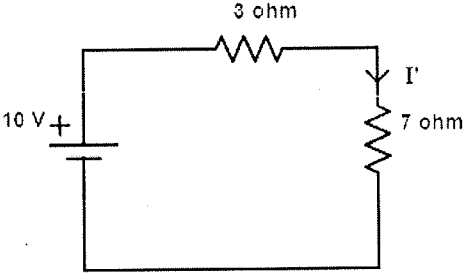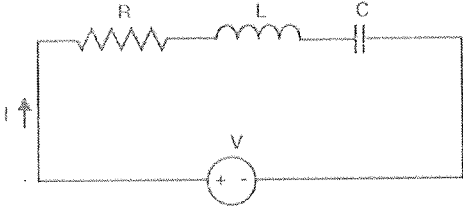IV	<p>Thevenin's voltage-3 marks Thevenin resistance-3 marks Thevenin equivalent circuit-1 mark</p>			
	<p>➤ Remove 7Ω and open the terminals</p>  <p>➤ $V_{th} = 6V + \text{voltage drop across } 3\Omega = 6 + 4 = 10\text{ V}$ To find R_{th}:-</p>  <p>➤ $R_{th} = 6 3 + 1 = 3\Omega$ ➤ Thevenin's equivalent is</p>  <p>➤ Current through 7 Ω, $I' = \frac{10}{10} = 1A$</p>	3	7	
V	<p>RLC circuit diagram-2 marks Explanation of different terms-2 marks Impedance triangle-1.5 marks Vector diagram-1.5 mark</p>			
	<p>RLC Series circuit</p>  <p>Impedance, $Z = \sqrt{R^2 + (X_L - X_C)^2}$ Current $I = V/Z$</p>	2	7	

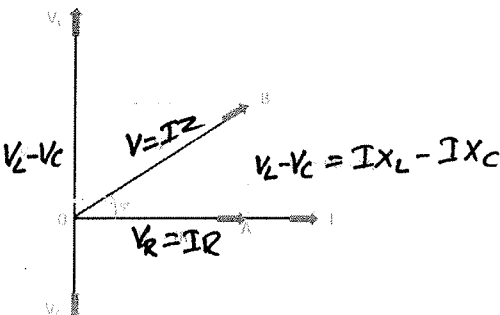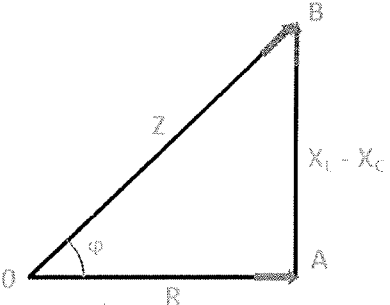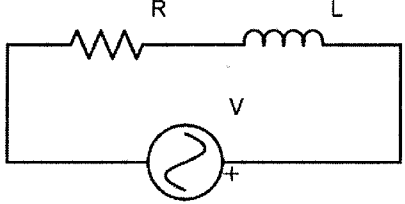
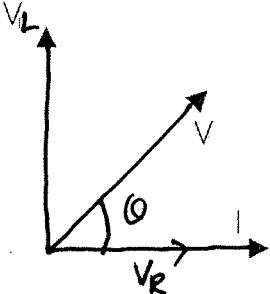
	<p>Power factor, $\cos \Phi = R/Z$</p> <p>Power $P = VI \cos \Phi$</p> <p><u>Vector diagram</u></p>  <p><u>Impedance triangle</u></p> 	2		
VI	<p><i>Circuit diagram-2 marks</i></p> <p><i>Vector diagram-1.5 marks</i></p> <p><i>Impedance triangle-1.5 marks</i></p> <p><i>Equation for Z, I, pf, P-2 marks</i></p>			
	  <p>Let $v = V_m \sin \omega t$ be the applied voltage</p> <p>$V_R = IR$, Voltage across resistor and is in phase with I</p> <p>$V_L = IX_L$, Voltage across inductor and is lead 90° with I</p>	3	7	

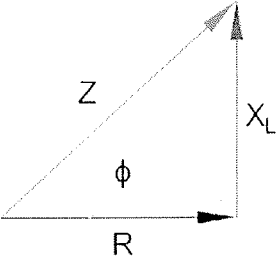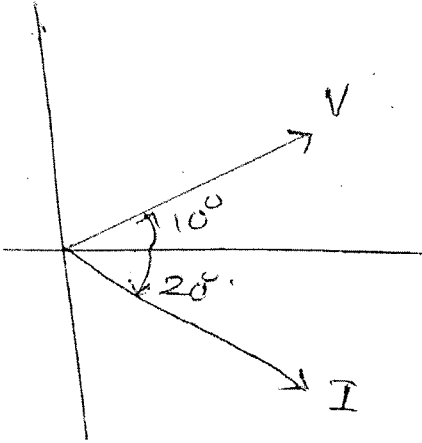	<p>$V = \overline{V}_R + \overline{V}_L$</p> <p>Impedance $Z = \sqrt{R^2 + X_L^2} = R + jX_L$</p> <p>Current $I = V/Z$</p> <p>Power factor = $\cos\Phi = V_R/V = IR/IZ = R/Z$</p> <p>Active Power = $VI \cos\Phi$</p> <p>Reactive Power = $VI \sin\Phi$</p> <p>Apparent Power = VI</p> <p><u>Impedance triangle</u></p> 	1		
VII	<p><i>Power factor-2 marks</i></p> <p><i>Power-3 marks</i></p> <p><i>Vector diagram-2 marks</i></p>			
	<p>$v(t) = 141.4 \sin(314t + 10^\circ)$</p> <p>$i(t) = 14.14 \sin(314t - 20^\circ)$</p> <p>(i) $\text{pf} = \cos\Phi = \cos(10 + 20) = 0.866 \text{ lag}$</p> <p>(ii) $P = VI \cos\Phi$</p> <p>$V = V_m/\sqrt{2} = 141.4/\sqrt{2} = 100\text{V}$</p> <p>$I = I_m/\sqrt{2} = 14.14/\sqrt{2} = 10\text{A}$</p> <p>$P = 100 \times 10 \times 0.866 = 866\text{W}$</p> <p>(iii) Vector diagram</p> 	2	7	
		3		
		2		

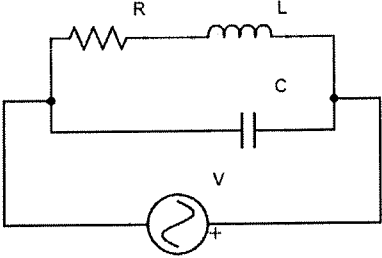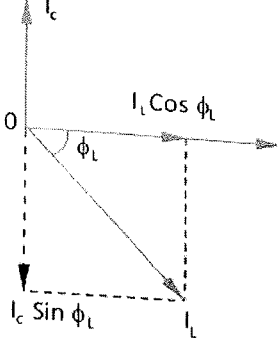VIII	<p style="text-align: right;">Z-1marks Current-1 mark Pf-1 mark Power-1 mark Voltage across R & C-2 marks</p> $X_C = \frac{1}{C\omega} = \frac{1}{2\pi \times 50 \times 100 \times 10^{-6}} = 31.83\Omega$ <p>(i) Impedance $Z = \sqrt{R^2 + (X_C)^2}$ =59.4Ω</p> <p>(i) Current, $I=V/Z= 1.68$ A</p> <p>(ii) $Pf=\cos\Phi=R/Z=0.842$ lead</p> <p>(iii) Power consumed= $VI \cos \Phi= 141.45W$</p> <p>(iv) Voltage Across R, $V_R= IR=84V$ Voltage across C, $V_c=IXC=53.76V$</p>	1 1 1 1 1 2	7	
IX	<p style="text-align: right;">RLC circuit-2 marks Resonant condition-3 mark Vector diagram- 2 marks</p> <p><u>Parallel RLC circuit</u></p>  <p><u>Vector diagram</u></p>  <p>Condition for resonance is the net reactive component become zero. $I_c - I_L \sin\Phi_L = 0 \dots\dots\dots 1$</p>	2 2	7	

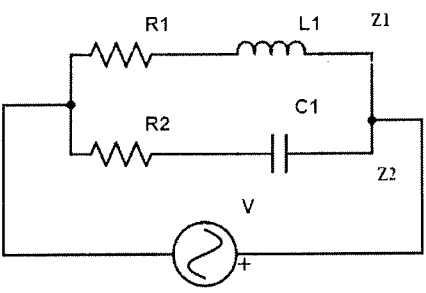	<p>At parallel resonance,</p> <ol style="list-style-type: none"> 1. The circuit impedance is maximum 2. Circuit current is minimum 3. Power factor is unity. <p>Now $I_L = V/Z$ $I_c = V/X_c$ $\sin\Phi_L = X_L/Z$ Eq.1 become , $X_L \cdot X_c = Z^2$</p> <p>Resonant frequency, $f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$</p>	3		
X	<p><i>Diagram-2 marks</i> <i>Explanation-5 marks</i></p>			
	<p>Admittance method Admittance, $Y=1/\text{Impedance}$. Consider a parallel circuit having two impedance Z_1 and Z_2.</p>  <p>For branch 1</p> $Z_1 = R_1 + jX_1 = \sqrt{R_1^2 + X_1^2}$ <p>Conductance, $g_1 = R_1/Z_1^2$ Susceptance, $b_1 = X_1/Z_1^2$ $Y_1 = g_1 - jb_1$</p> <p>For branch 2</p> $Z_2 = R_2 - jX_2 = \sqrt{R_2^2 + X_2^2}$ <p>Conductance, $g_2 = R_2/Z_2^2$ Suceptance, $b_2 = X_2/Z_2^2$ $Y_2 = g_2 + jb_2$</p>	<p style="text-align: center;">1</p> <p style="text-align: center;">2</p> <p style="text-align: center;">4</p>	7	


	<p>Total admittance $Y=Y_1+Y_2$</p> <p>Current $I= VY$</p> <p>Power factor $\cos\Phi= G/Y$</p>			
XI	<p style="text-align: right;"><i>Line current- 2 marks</i></p> <p style="text-align: right;"><i>Power-2 marks</i></p> <p style="text-align: right;"><i>Reactive power-2 mark</i></p> <p style="text-align: right;"><i>Apparent power-1 mark</i></p>			
	<p>$Z=8+j6$, $V_L=230$ V, star</p> <p>$V_{ph}=V_L/\sqrt{3}=132.8$V</p> <p>$Z_{ph}=\sqrt{8^2 + 6^2} = 10\Omega$</p> <p>(i) Current, $I_{ph}=V_{ph}/Z_{ph}= 13.28$A.</p> <p>Line current, $I_L=I_p=13.28$A.</p> <p>(ii) Power=$\sqrt{3} V_L I_L \cos\Phi$</p> <p>$Pf=\cos\Phi=R/Z=8/10=0.8$</p> <p>$P=4232$W</p> <p>(iii) Reactive Power, $Q=\sqrt{3} V_L I_L \sin\Phi=3174$ VAR</p> <p>(iv) Total kVA=$\sqrt{3} V_L I_L =5290$VA</p>	<p>1</p> <p>2</p> <p>2</p> <p>1</p> <p>1</p>	7	
XII	<p>$V_{ph}=V_L=400$V, $I=10$A $\cos\Phi=0.7$</p> <p>(i) $I_{ph}=I_L/\sqrt{3}=5.77$A</p> <p>(ii) $Z_{ph}= V_{ph}/I_{ph}=69.28\Omega$</p> <p>(iii) $R_{ph}=Z_{ph} \cos\Phi=48.49\Omega$</p> <p style="padding-left: 40px;">$X_{ph}=\sqrt{Z^2 - R^2} = 49.48\Omega$</p> <p>(iv) Active Power, $P=\sqrt{3} V_L I_L \cos\Phi=4850$W</p> <p>(v) Reactive power, $Q=\sqrt{3} V_L I_L \sin\Phi=4948$ VAR</p> <p>(vi) Apparent Power, $S=\sqrt{3} V_L I_L=6928.2$VA</p>	<p>1</p> <p>1</p> <p>2</p> <p>1</p> <p>1</p> <p>1</p>	7	
XIII	<i>Any seven points -1 mark each</i>			

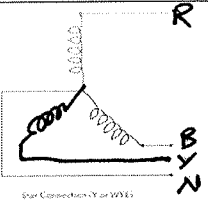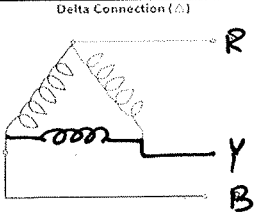Si. No.	Star(Y) connected system	Delta(Δ)connected system
1	Neutral point is there and it can be earthed.	No neutral point
2	$V_L = \sqrt{3} V_{ph}$	$V_L = V_{ph}$
3	$I_L = I_{ph}$	$I_L = \sqrt{3} I_{ph}$
4	3 phase three wire and 3 phase 4 wire system	Only 3-phase 3-wire system
5	Low insulation is required as phase voltage is low	Heavy insulation is required as phase voltage=line voltage
6		
7	Usually star connection is used in the transmission and distribution.	Delta is used in the Distribution.
8	Three phase power, $P = \sqrt{3} V_L I_L \cos \theta$	Three phase power, $P = \sqrt{3} V_L I_L \cos \theta$

XIV

*Diagram-1 mark
Phasor diagram-3 marks
Explanation-3 marks*

Star Connected Three phase system

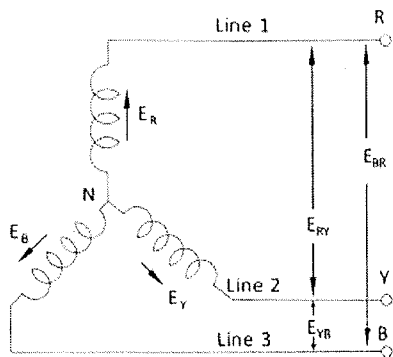

Let


E_R, E_Y and $E_B =$ phase voltages of R, Y, B phases and are equal to ' E_{ph} '

E_{RY}, E_{YB} and $E_{BR} =$ line voltages of RY, YB, BR respectively and are equal to ' E_L '

Vector Diagram

1

7

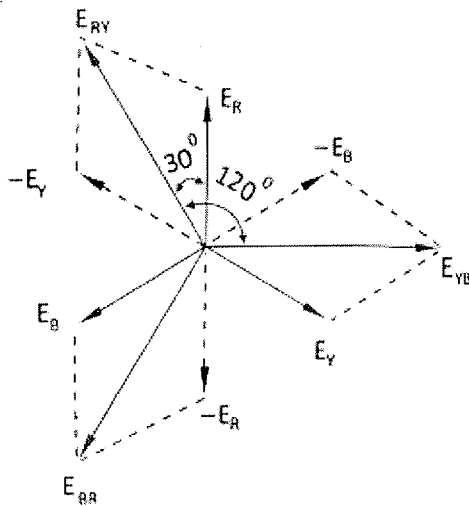

2

The p.d. between outers R and Y is

$$\begin{aligned}
 E_{Ry} &= E_R - E_y && \text{..... Vector difference} \\
 &= E_R + (-E_y) && \text{..... Vector sum.}
 \end{aligned}$$

4

The phase angle between vectors E_R and $(-E_y)$ or E_y reversed is 60° .

\therefore From vector diagram shown in Fig. 4.9 (b).

$$\begin{aligned}
 E_{Ry} &= \sqrt{E_R^2 + E_y^2 + 2E_R E_y \cos 60^\circ} \\
 &= \sqrt{E_{ph}^2 + E_{ph}^2 + 2E_{ph} \cdot E_{ph} \times \frac{1}{2}} \\
 \therefore E_R &= E_y = E_B = E_{ph} \text{ for a balanced system} \\
 &= \sqrt{3 E_{ph}^2} = \sqrt{3} E_{ph}^*
 \end{aligned}$$

Similarly p.d. between outers Y and B is

$$E_{yB} = E_y - E_B = \sqrt{3} E_{ph}.$$

and p.d. between outers B and R is

$$E_{BR} = E_B - E_R = \sqrt{3} E_{ph}.$$

Hence, in balanced star connected system

$$E_{Ry} = E_{yB} = E_{BR} = \boxed{E_L = \sqrt{3} E_{ph}}$$